



CPEN 311: Digital Systems Design

Finite State Machines (Control Circuits)

Learning Objectives

- Distinction between datapath and control
 - Control is usually built using finite state machine (FSM)
- Difference between Moore machine and Mealy machine
- How to design Moore machine
- How to design Mealy machine

FSM Design Summary

Manually creating an FSM involves the following 6 steps:


1. Generate state diagram
2. Generate state table
3. State assignment
4. Truth tables
5. Karnaugh maps and logic equations
6. Circuit diagram

Finite State Machines

- Logic circuits generally divided into two parts
 - Datapath that does the “arithmetic”
 - adders, ALUs, muxes, registers
 - Control logic
 - Arranges the “sequencing” or steering of data in datapath
 - Often designed as a finite state machine (FSM)
- Finite State Machine
 - A “program” or set of “instructions” for the datapath
 - Eg: “do step 1, do step 2, move data here, if(...) repeat”
- Example FSM: 2-bit Counter (0, 1, 2, 3, 0, 1, ...)
 - After reset: count = 0
 - Each clock cycle: count = count + 1

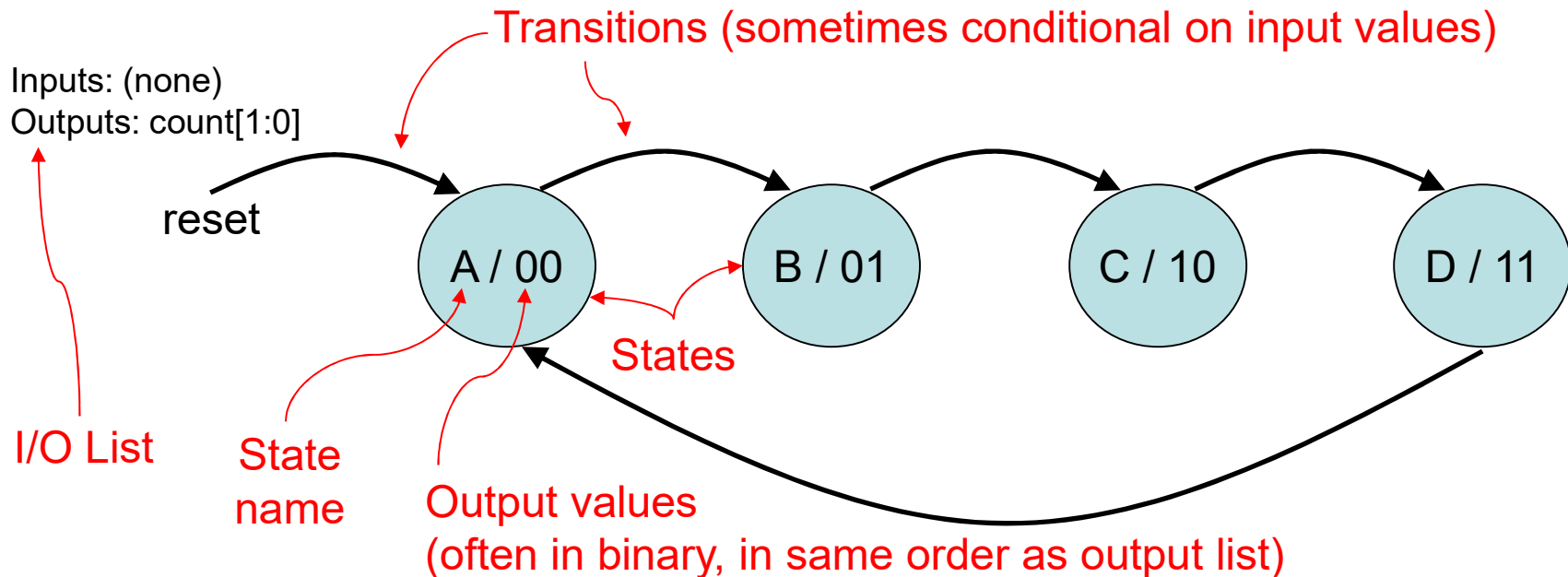Example FSM 1


- 2-bit Counter (0, 1, 2, 3, 0, 1, 2, ...)
 - Reset: count = 0. Each cycle: count++.



- Only 1 state active at a time
 - Eg: state A is active for 1 cycle after reset, state B is active for 1 cycle after A, etc.
 - Always designate a “reset” state
- Transitions occur on every clock edge
 - Each state always has an outward transition (can be to self)
 - Transition can be conditional upon an input value

 Example FSM 2

- 2-bit **Conditional Saturating** Counter (0, 1, 2, 3, 3, ...)
 - Reset: count = 0. Each cycle: **if(up==1 & count<3)** count++.




- Transitions labeled with conditions
 - up=0: transition to same state
 - up=1: transition to next state
- For each state
 - Outgoing transitions for **all possible input values**
 - If any input value is omitted, what should be the next state?
 - Outgoing transitions have **mutually exclusive conditions**
 - Can only follow 1 outgoing transition (“deterministic finite automata” or DFA)
- Like outputs, inputs can have multiple signals or multiple bits
 - Clearly define an order

Example: FSM as Logic

Example Problem

- Develop a circuit with input **w**, output **z**, reset, clock
- Output **z=1** if previous 2 clock cycles both see **w=1**, otherwise **z=0**

1. Generate state diagram

 

2. Generate state table

Present State	Next State		Outputs Z
	W=0	W=1	
A*	A	B	0
B	A	C	0
C	A	C	1

* Reset state

State Table

Deriving Logic Equations

Given State Table, derive logic equations

Present State	Next State		Outputs z
	w=0	w=1	
A*	A	B	0
B	A	C	0
C	A	C	1

State Table
(before state assignment)

3. State assignment: assign binary values to states

- A=00, B=01, C=10 (other assignments possible, eg A=10, B=01, C=11)

Present State	Next State		Outputs z
	w=0	w=1	
00*	00	01	0
01	00	10	0
10	00	10	1
11	xx	xx	x

State Table
(after state assignment)

- Notice 11 isn't used by any state, but we must add it to table
 - Why?
 - Use xx = don't care values. Why?

Deriving Logic Equations

4. Derive truth tables after state assignment

- PS = present state, signals y2 y1
- NS = next state, signals Y2 Y1

PS	NS: Y2 Y1		Outputs
y2 y1	w=0	w=1	z
00*	00	01	0
01	00	10	0
10	00	10	1
11	xx	xx	x

State Table
(after state assignment)



Inputs	Output Y2	
y2 y1	w=0	w=1
00	0	0
01	0	1
10	0	1
11	x	x

Inputs	Output Y1	
y2 y1	w=0	w=1
00	0	1
01	0	0
10	0	0
11	x	x

Inputs	Output
y2 y1	z
00	0
01	0
10	1
11	x

Truth Tables

(ignore reset for now; don't forget that reset must initialize y2y1 = 00)

Deriving Logic Equations

5. Derive logic equations and Karnaugh maps from truth tables

- PS = present state, signals y2 y1
- NS = next state, signals Y2 Y1

Inputs		Output Y2		Inputs		Output Y1		Inputs		Output z
y2	y1	w=0	w=1	y2	y1	w=0	w=1	y2	y1	
0	0	0	0	0	0	0	1	0	0	0
0	1	0	1	0	1	0	0	0	1	0
1	0	0	1	1	0	0	0	1	0	1
1	1	x	x	1	1	x	x	1	1	x

Truth Tables

Signal Y2

		w	
		0	1
00	y2y1	0	0
01		0	1
11		x	x
10		0	1

Signal Y1

		w	
		0	1
00	y2y1	0	1
01		0	0
11		x	x
10		0	0

Signal z

		y1	
		0	1
0	y2	0	0
1		1	x

Karnaugh Maps

$$Y2 = w \& y1 + w \& y2 \\ = w \& (y1 + y2)$$

$$Y1 = w \& !y2 \& !y1$$

$$z = y2$$

Logic Equations

Notice 1: next state Y2, Y1 is a function of present state y2, y1 and input w

Notice 2: output z is a function of present state y2 (not input w)

Circuit Diagram


6. Derive circuit diagram from logic equations

$$Y2 = w \& (y1 + y2)$$

$$Y1 = w \& !y2 \& !y1$$

$$z = y2$$

Logic Equations

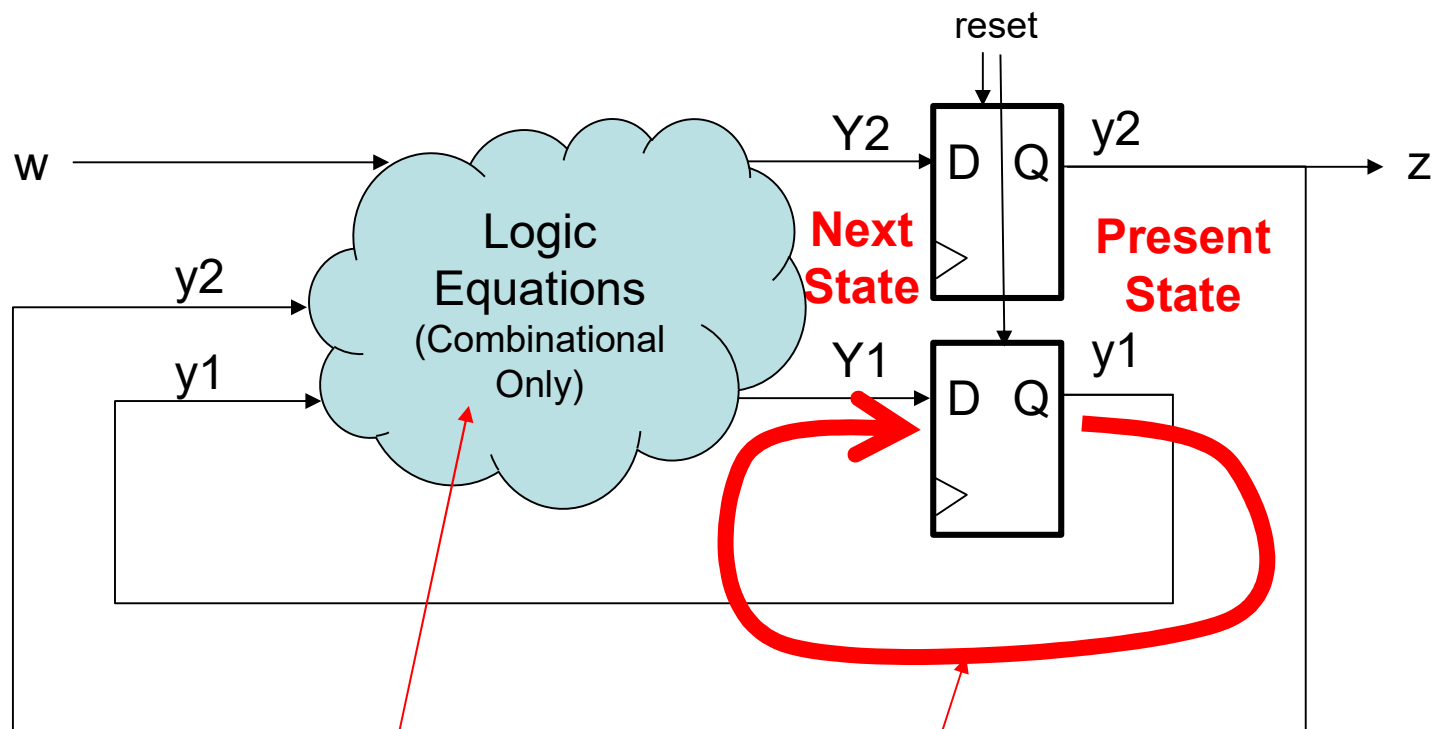

Circuit


**Combinational logic
never has loops**

**Sequential logic
can have loops!**

Why and how does this work?

- 1) Clock adds time delay from $y1 \rightarrow Y1$
- 2) Both $y1$ and $y2$ change at same time (on clock edge); $Y2$, $Y1$ stable before edge

General FSM Model: Moore Machine

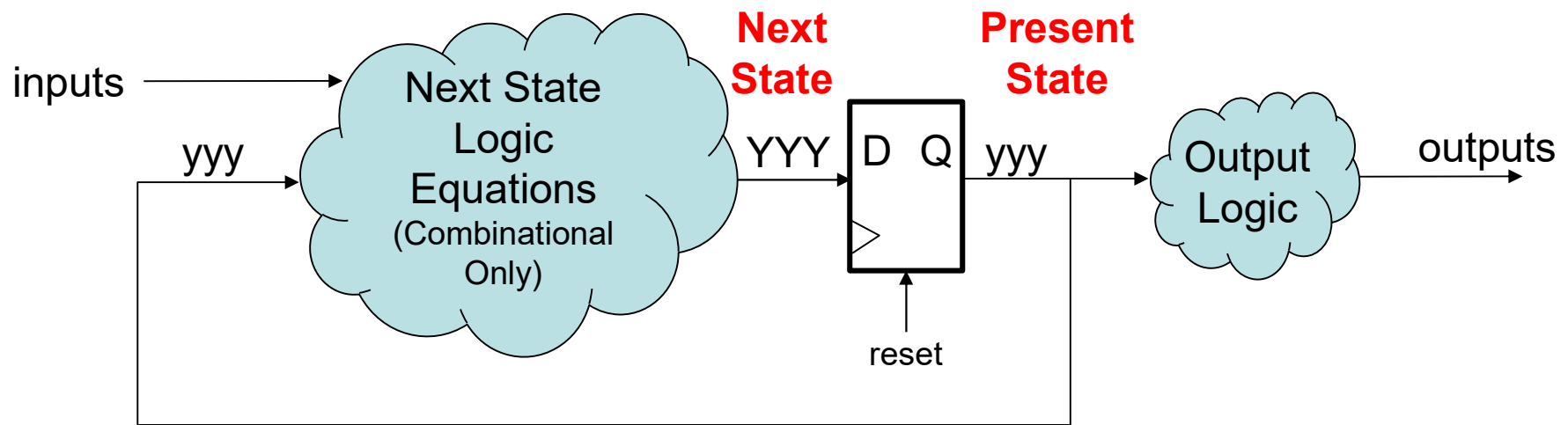

General model of **Moore Machine** FSM model

- Outputs are **only** a function of present state
 - **By design** because we wrote output values inside state bubbles
 - Inputs never appear in equation for outputs

FSM Design Summary

Manually creating an FSM involves the following 6 steps:

1. Generate state diagram
2. Generate state table
3. State assignment
4. Truth tables
5. Karnaugh maps and logic equations
6. Circuit diagram

You DO NOT want to enter the circuit diagram in Verilog

- Instead, you can replace steps 2..6 with:
2. Generate state-transition code in Verilog

Quartus will happily synthesize (& optimize) the required logic for you

Be sure to follow the Moore model (outputs depend on state only)!

Moore FSM Example


Example Problem

- Design the Moore FSM for a serial adder (implies reset, clock)
- Inputs **a**, **b** presented serially (LSB first, 1 bit per clock cycle)
- Output **s** is **a+b**, presented serially (LSB first)

$$\begin{array}{r} \text{Full} \quad a \\ \text{adder:} \quad b \\ \quad + c_i \\ \hline C_o \quad S \end{array}$$

$$S = a \text{ XOR } b \text{ XOR } c_i$$
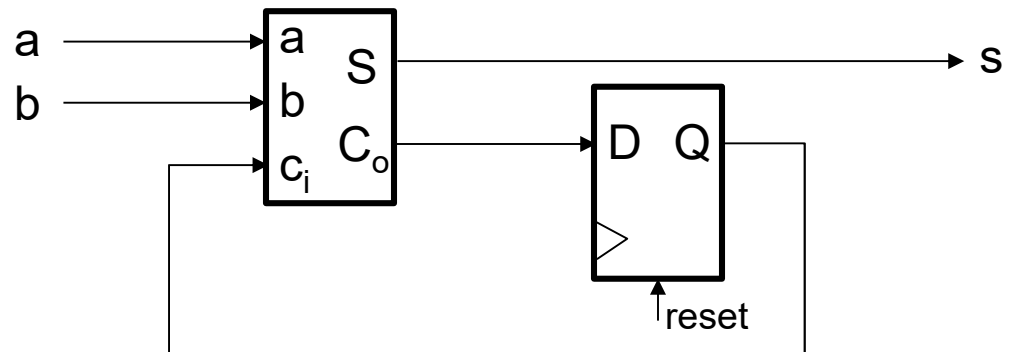
$$C_o = a \cdot b + a \cdot c_i + b \cdot c_i$$




We intuitively know the solution...


- Full adder to compute sum (**S**) and carry-out (**C_o**)
- Use a flip-flop to connect carry-out to carry-in on the next clock cycle
- Output **s** is function of inputs **a**, **b** and present state → not a Moore FSM

How to derive as Moore FSM?

Moore FSM for Serial Adder

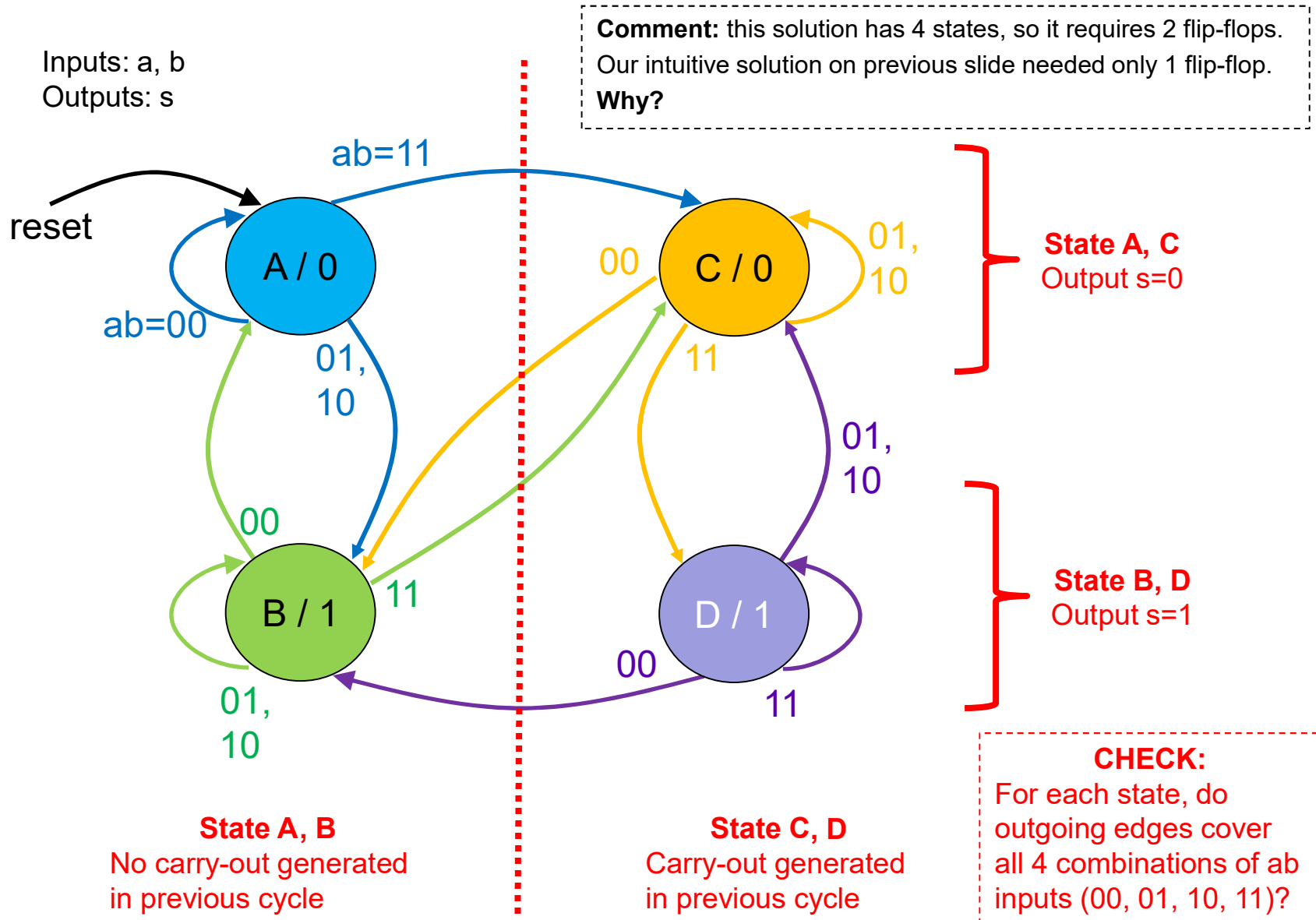

Moore FSM for Serial Adder

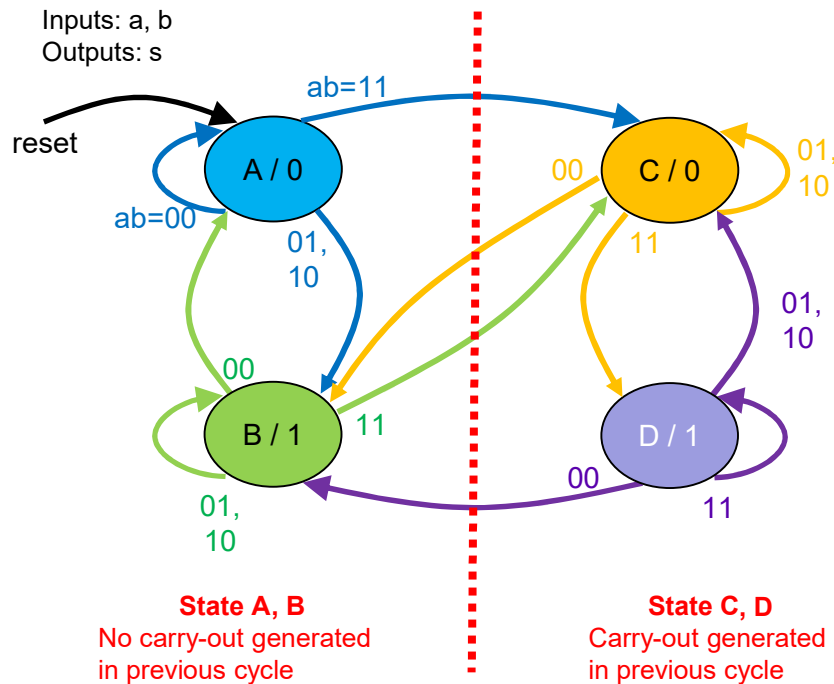

STEPS:

1. State diagram
2. State table
3. State assignment
4. Truth table
5. K-map and logic
6. Circuit

$Y1 = a \text{ XOR } b \text{ XOR } y2$
 $Y2 = a.b + a.y2 + b.y2$
 $s = y1$

- Verify the above!
- Notice that $c_i = y2$
- Then, if we remove FF for $y1$, we get the intuitive solution!

Present State	Next State				Output s
	ab=00	01	11	10	
A*	A	B	C	B	0
B	A	B	C	B	1
C	B	C	D	C	0
D	B	C	D	C	1


* Reset state

State assignment:

A=00, B=01, C=10, D=11

Present State y2y1	Next State Y2Y1				Output s
	ab=00	01	11	10	
00	00	01	10	01	0
01	00	01	10	01	1
11	01	10	11	10	1
10	01	10	11	10	0

General FSM Model: Mealy Machine

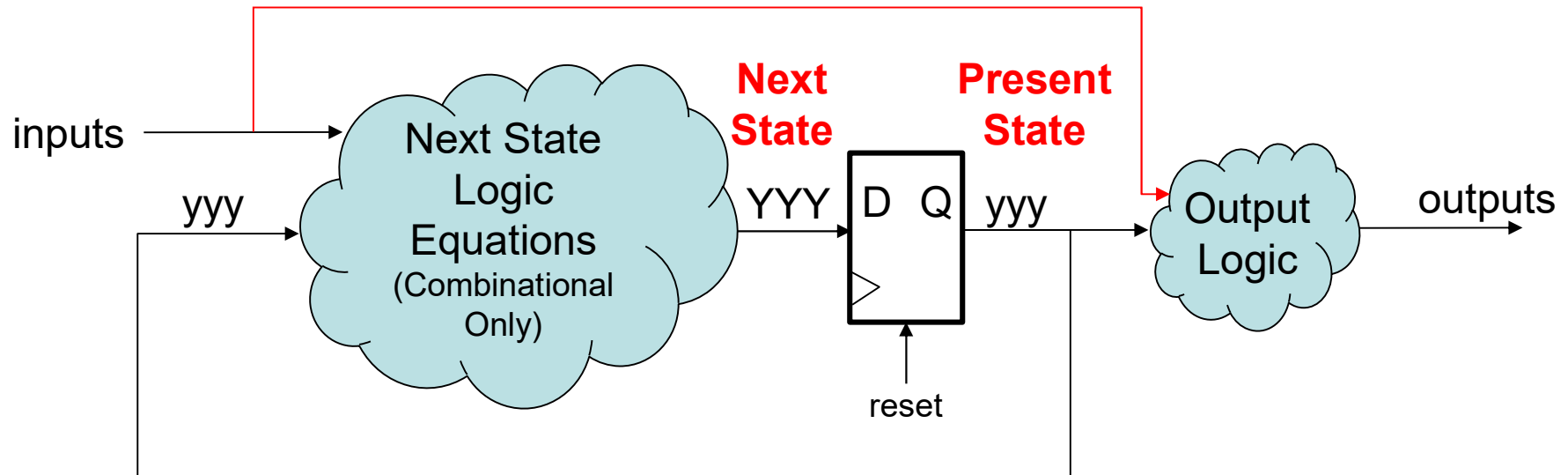

General model of **Mealy Machine** FSM model

- Outputs are a function of **both** state **and** inputs
 - **By design** because **we will write output values on transitions**
 - Changes to inputs may cause immediate change to outputs
- Typical properties of Mealy...
 - has fewer states than Moore (why?)
 - logic for outputs is more complex, produces glitchy outputs
 - next-state logic is more complex, slower clock frequency
 - often takes fewer clock cycles to do a task


Mealy FSM Example

Example Problem

- Design the Mealy FSM for a serial adder (implies reset, clock)
- Inputs **a**, **b** presented serially (LSB first, 1 bit per clock cycle)
- Output **s** is **a+b**, presented serially (LSB first)

(this is the same as before, except use Mealy model instead of Moore)

Mealy FSM for Serial Adder

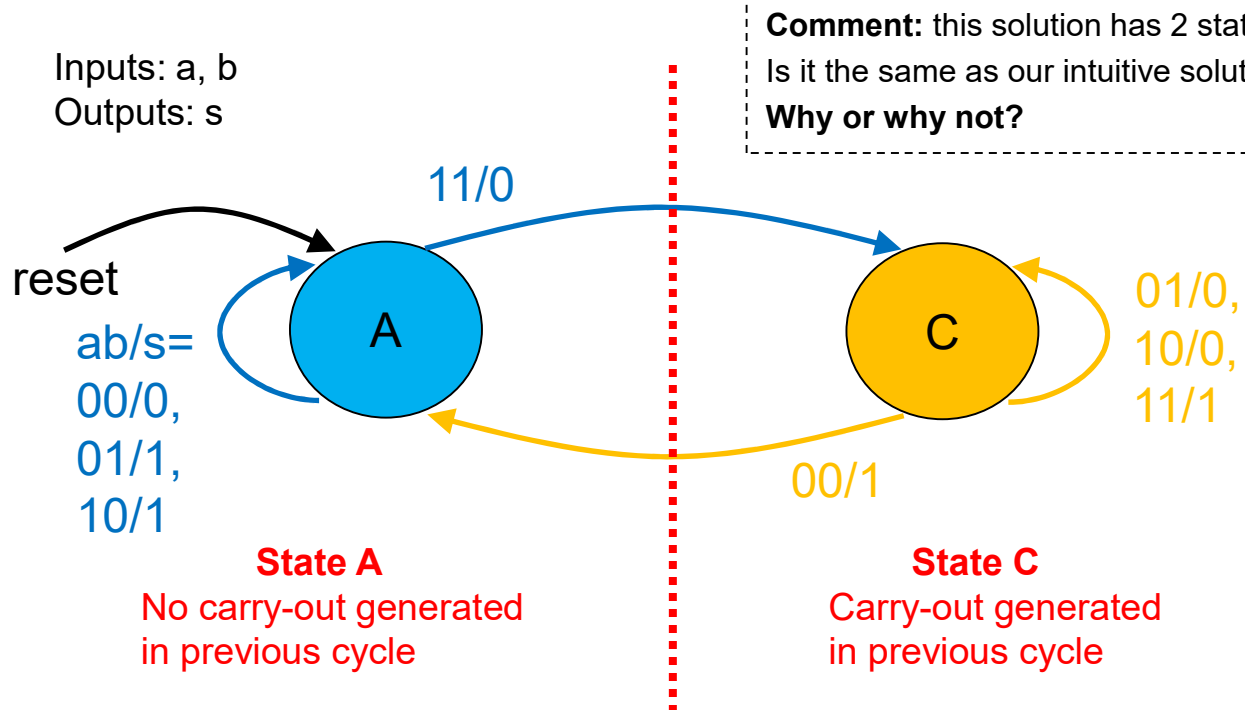

STEPS:

1. State diagram
2. State table
3. State assignment
4. Truth table
5. K-map and logic
6. Circuit


Notice

For each state, all possible input values are labelled on transitions.

For each possible input value, in each state, an output value is specified.

Output values can change when staying in the same state.

Mealy FSM Example

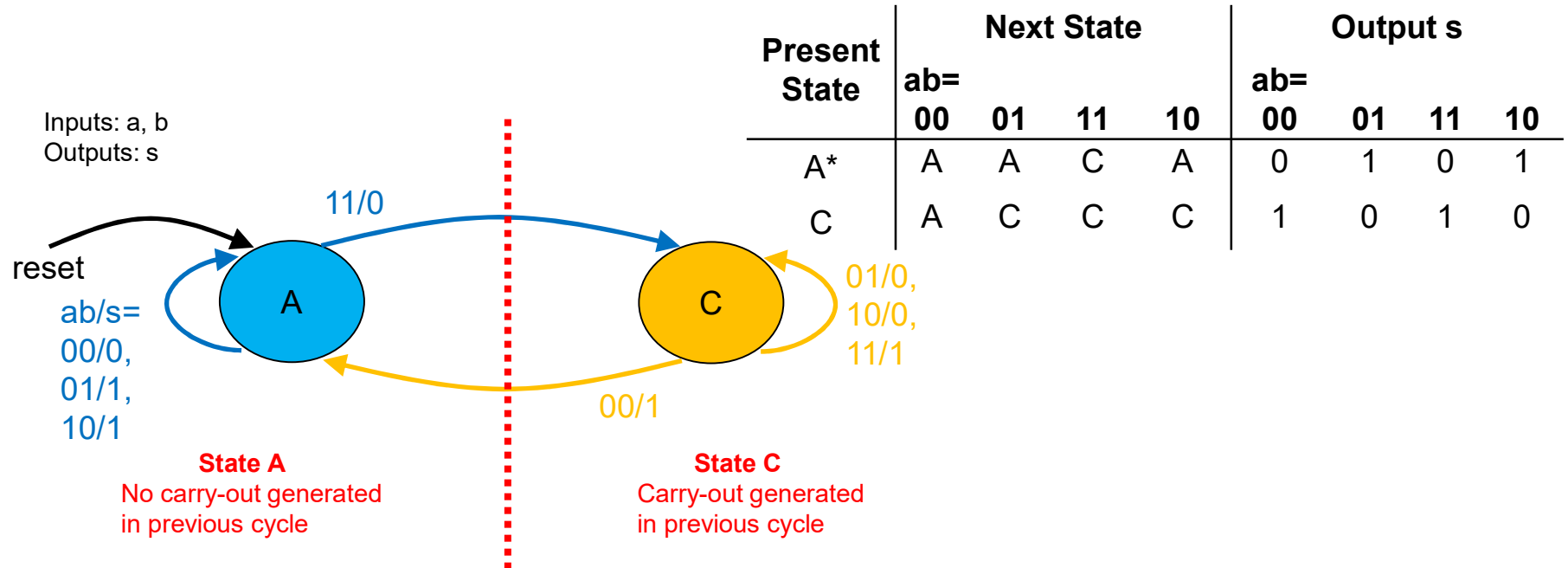

State assignment: A=0, C=1

STEPS:

1. State diagram
2. State table
3. State assignment
4. Truth table
5. K-map and logic
6. Circuit

$Y2 = a.b + a.y2 + b.y2$
 $s = a \text{ XOR } b \text{ XOR } y2$

- Verify the above!
- Notice that $c_i = y2$
- This is the same as the intuitive solution!

Present State y2	Next State Y2				Output s			
	ab=00	01	11	10	ab=00	01	11	10
0	0	0	1	0	0	1	0	1
1	0	1	1	1	1	0	1	0

Mealy vs. Moore

- Moore is usually easier to design
 - But it usually has more states in total
 - But it can take more states to complete a task
 - **Moore** has **more** states ← way to remember difference
 - Outputs are delayed until next clock cycle
 - Outputs are stable (no glitches) entire clock cycle
- Mealy advantages
 - Outputs can change immediately (glitches)
 - Fewer states in total, since outputs can depend upon inputs
 - Completes a task in fewer clock cycles
 - Faster than Moore?
 - But next-state logic can be more complex (slower clock speed)
 - Slower than Moore?
- Hybrids are possible...
 - Some outputs function of state only
 - Some outputs function of state+inputs
- Serial adder examples: Mealy solution looks simpler than Moore
 - Only because it's a trivial example
 - Usually opposite is true!

Summary

- Use FSMs to control a datapath
 - Always sequential logic
 - Has memory of past inputs!
 - Has loops (new state is function of current state)
 - Moore machine ← preferred method for novices
 - Outputs function of state only
 - More total states (one state for every possible output value)
 - Outputs stable entire clock cycle
 - Mealy machine
 - Outputs function of state and inputs
 - Fewer total states (output values on transition conditions instead of states)
 - Fewer states to finish a task (outputs produced sooner)
 - Outputs may glitch, change when inputs change
- Design process
 - Two steps with Verilog
 - Six steps when done manually

Exercises 1

1. Design a Moore FSM that has an input **w** and an output **z**. The machine is a sequence detector that produces **z=1** when the previous two values of **w** were 00 or 11; otherwise **z=0**.
2. Write the Verilog code for the Moore FSM.
3. Repeat the design for a Mealy FSM.
4. Write the Verilog code for the Mealy FSM.

Exercises 2

5. Complete the design process for the following two FSMs. Which one is a Mealy machine? Which one is a Moore machine?

