



CPEN 311: Digital Systems Design

Circuit Timing: Part 2: Practical Issues

Learning Objectives

1. Understand what timing closure is and why it is difficult
2. Understand how pipelining can help with timing closure
3. Understand retiming and be able to apply it to a circuit
4. Be able to discuss the effects of clock skew
5. Understand what a PLL is used for
6. Understand the cause and impact of glitches caused by unequal combinational path delays

Timing Closure

Timing Closure: Ensuring your design meets timing constraints

So far you have been compiling and just hoping it runs at the required speed
(eg. If you are using CLOCK_50, the critical path ≤ 20 ns)

That was fine for these simple labs, but for complex designs, a simple compile may not lead to you meet your timing constraints.

The screenshot displays the Quartus II IDE interface. The 'Table of Contents' on the left lists various reports, with 'Fmax Summary' selected under the 'Slow 1200mV 85C Model' folder. A red arrow points from this entry to the 'Slow 1200mV 85C Model Fmax Summary' report window. The report window contains a table with the following data:

	Fmax	Restricted Fmax	Clock Name	Note
1	180.38 MHz	180.38 MHz	clk	


Below the table, a text box explains: "This panel reports FMAX for every clock in the design, regardless of the user-specified clock periods. FMAX is only computed for paths where the source and destination registers or ports are driven by the same clock. Paths of different clocks, including generated clocks, are ignored. For paths between a clock and its inversion, FMAX is computed as if the rising and falling edges are scaled along with FMAX, such that the duty cycle (in terms of a percentage) is maintained. Altera recommends that you always use clock constraints and other slack reports for..."

The Messages window at the bottom shows the following log entries:

- Info (204019): Generated file lab3_6_1200mv_0c_vhd_slow.sdo in folder "/Desktop/temp2/simulation/modelsim/" f
- Info (204019): Generated file lab3_min_1200mv_0c_vhd_fast.sdo in folder "/Desktop/temp2/simulation/modelsim/"
- Info (204019): Generated file lab3_vhd.sdo in folder "/Desktop/temp2/simulation/modelsim/" for EDA simulation
- Info: Quartus II 32-bit EDA Netlist Writer was successful. 0 errors, 0 warnings
- Info (293026): Skipped module PowerPlay Power Analyzer due to the assignment FLOW_ENABLE_POWER_ANALYZER
- Info (293000): Quartus II Full Compilation was successful. 0 errors, 44 warnings

Based on register-register delays

From my implementation of the lab:

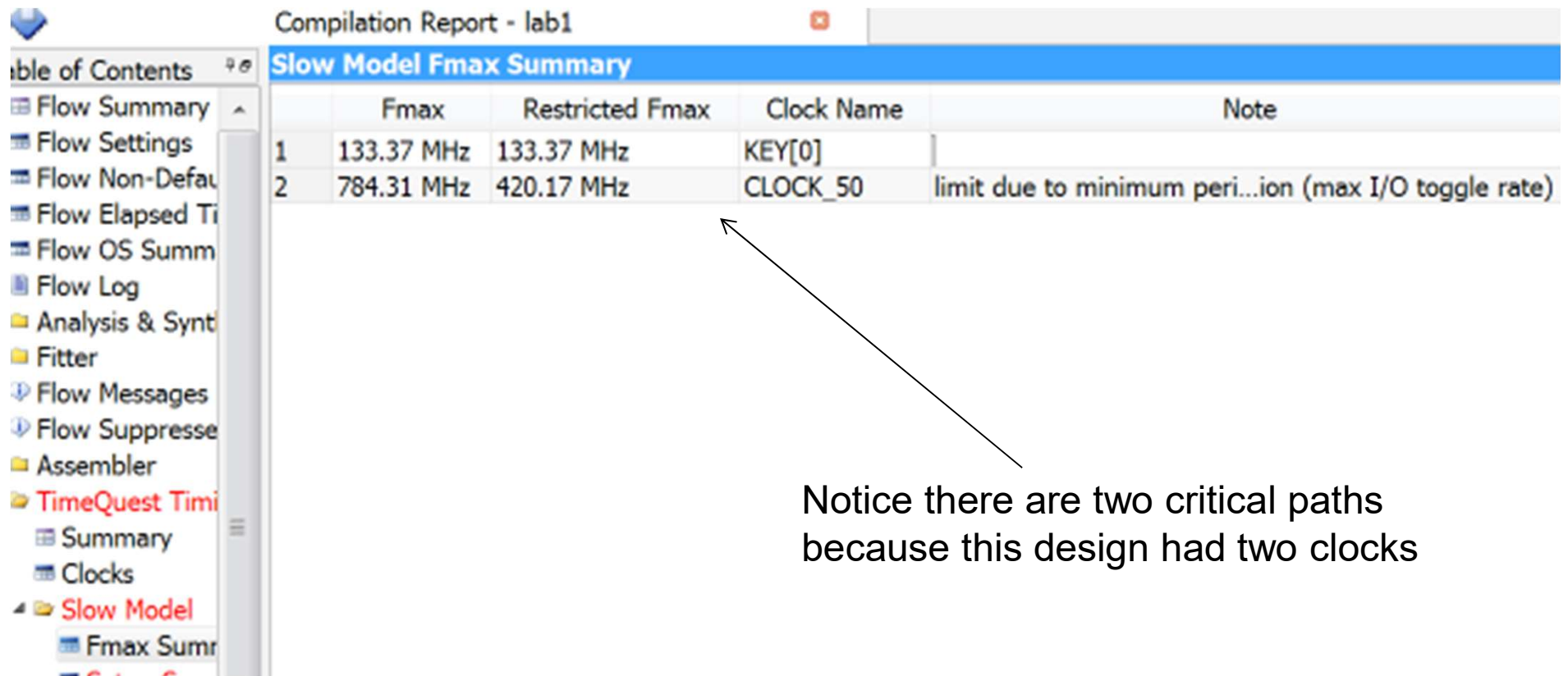

Compilation Report - lab1

Slow Model Fmax Summary

	Fmax	Restricted Fmax	Clock Name	Note
1	133.37 MHz	133.37 MHz	KEY[0]	
2	784.31 MHz	420.17 MHz	CLOCK_50	limit due to minimum period (max I/O toggle rate)


Notice there are two critical paths because this design had two clocks

Fmax means the maximum frequency the circuit can run at

Timing Constraints in Quartus II

You can specify a desired **target clock frequency**
aka **Timing Constraint**

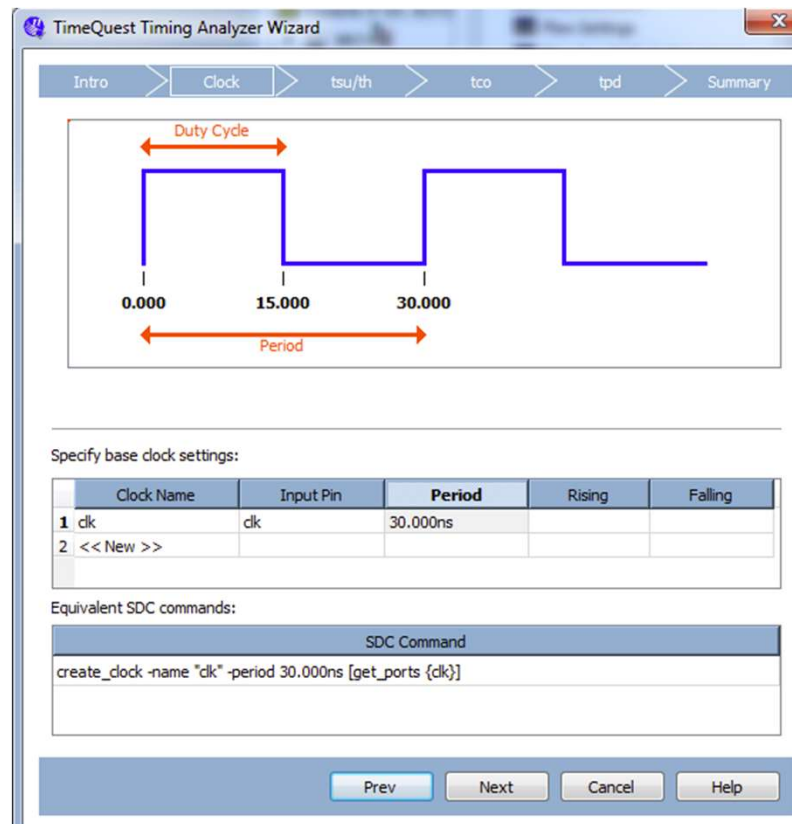Assignments Menu → Timing Analysis Wizard



Quartus Timing Optimization

- Tries to meet your desired clock frequency
 - By default, an unachievable value (eg, 1GHz)
 - Better to specify actual target (eg, 50MHz)
- May not meet target
 - Limited by logic + routing delays in FPGA

When you ask for...

slow clock frequency

smaller circuits → optimize total number of logic gates

fast clock frequency

larger circuit → optimize number of logic gates along path

All about tradeoffs!


Tradeoffs: Lab 1

Experiments conducted on a DE2 board:

Scenario	Achieved Fmax	Area of Circuit
No explicit timing constraints (1 GHz)	133 MHz	148 Logic Elements
Timing constraint of 130 MHz	130 MHz	143 Logic Elements
Timing constraint of 10 MHz	112 MHz	135 Logic Elements

The next few slides are meant as a kind of “case study” so you understand what timing closure is all about.

Timing Violations

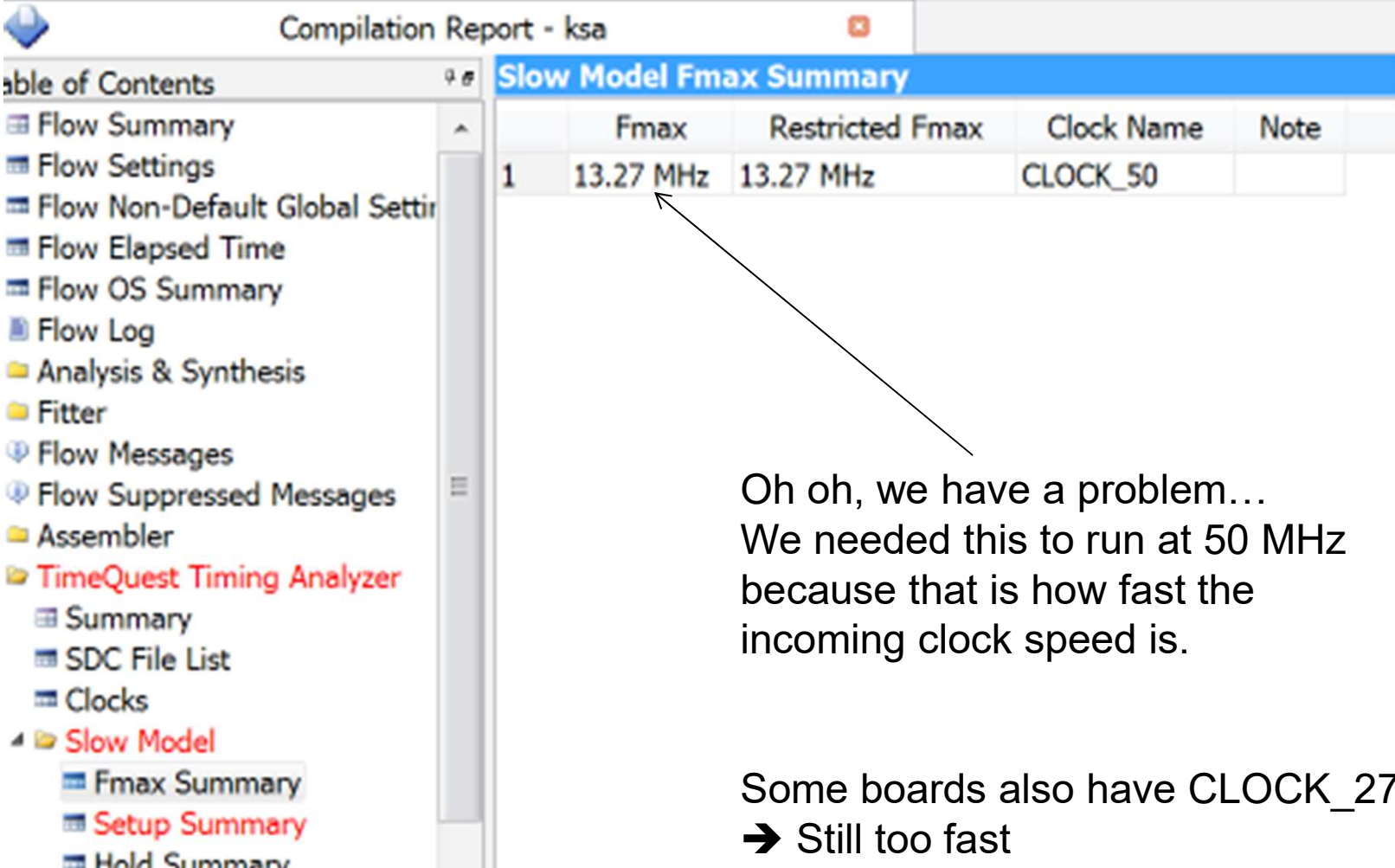


The screenshot shows the 'Compilation Report - ksa' window. The left sidebar contains a 'Table of Contents' with various report sections. The 'Slow Model' section is expanded, showing 'Fmax Summary', 'Setup Summary', and 'Hold Summary'. The 'Fmax Summary' table is displayed in the main pane, showing a violation for 'CLOCK_50' at 13.27 MHz. An arrow points from the text 'Oh oh, we have a problem...' to the '13.27 MHz' value in the table.

	Fmax	Restricted Fmax	Clock Name	Note
1	13.27 MHz	13.27 MHz	CLOCK_50	

Oh oh, we have a problem...
We needed this to run at 50 MHz
because that is how fast the
incoming clock speed is.

Some boards also have CLOCK_27
➔ Still too fast

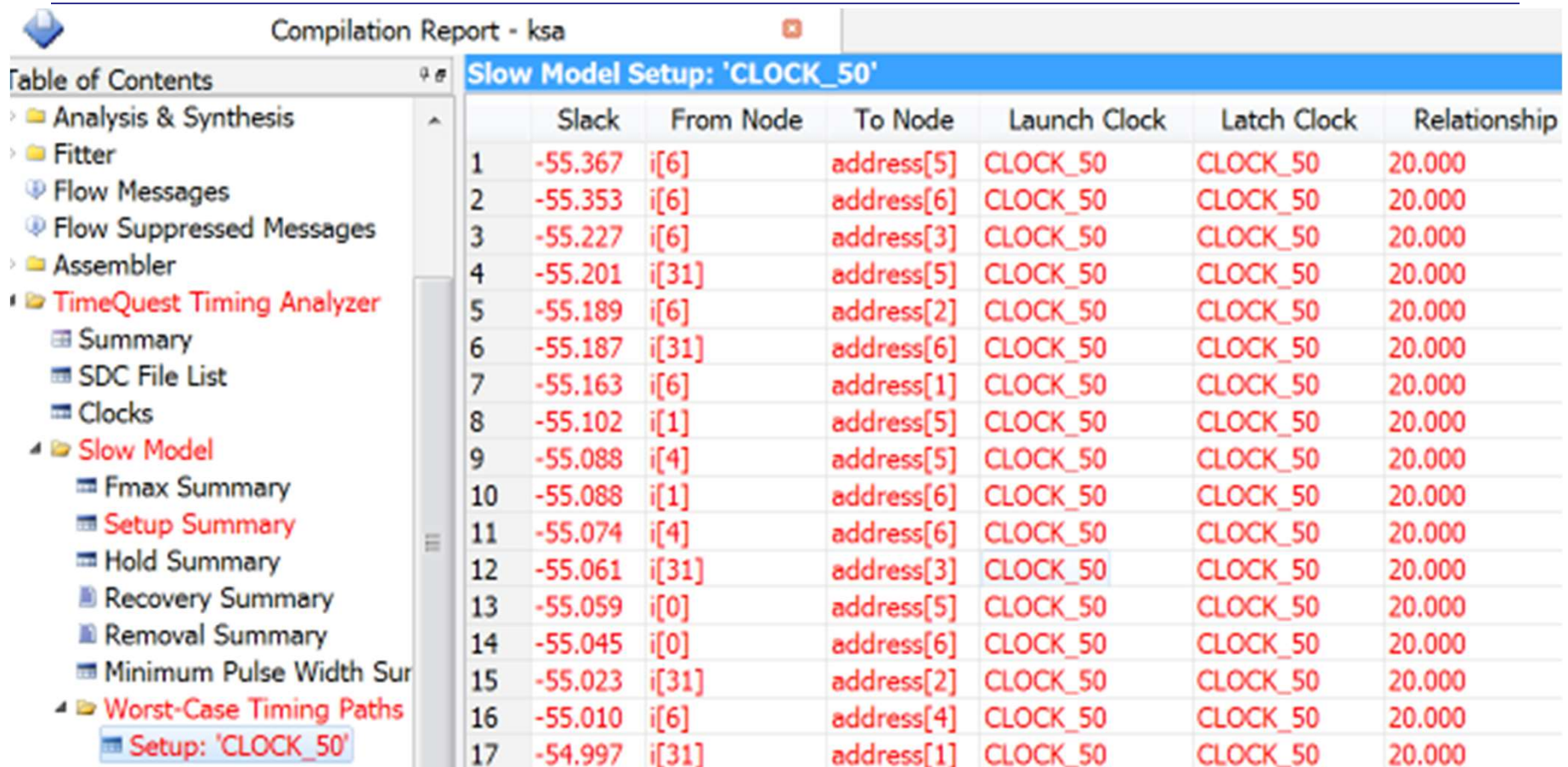Let's investigate: Worst-Case Timing Paths



The screenshot shows the 'Compilation Report - ksa' window. On the left is a 'Table of Contents' tree with the following structure:

- Analysis & Synthesis
- Fitter
 - Flow Messages
 - Flow Suppressed Messages
- Assembler
- TimeQuest Timing Analyzer**
 - Summary
 - SDC File List
 - Clocks
 - Slow Model**
 - Fmax Summary
 - Setup Summary**
 - Hold Summary
 - Recovery Summary
 - Removal Summary
 - Minimum Pulse Width Sur
 - Worst-Case Timing Paths**
 - Setup: 'CLOCK_50'**

The main table displays the 'Slow Model Setup: 'CLOCK_50'' results. It has 7 columns: an index, Slack, From Node, To Node, Launch Clock, Latch Clock, and Relationship. The data is as follows:


	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship
1	-55.367	i[6]	address[5]	CLOCK_50	CLOCK_50	20.000
2	-55.353	i[6]	address[6]	CLOCK_50	CLOCK_50	20.000
3	-55.227	i[6]	address[3]	CLOCK_50	CLOCK_50	20.000
4	-55.201	i[31]	address[5]	CLOCK_50	CLOCK_50	20.000
5	-55.189	i[6]	address[2]	CLOCK_50	CLOCK_50	20.000
6	-55.187	i[31]	address[6]	CLOCK_50	CLOCK_50	20.000
7	-55.163	i[6]	address[1]	CLOCK_50	CLOCK_50	20.000
8	-55.102	i[1]	address[5]	CLOCK_50	CLOCK_50	20.000
9	-55.088	i[4]	address[5]	CLOCK_50	CLOCK_50	20.000
10	-55.088	i[1]	address[6]	CLOCK_50	CLOCK_50	20.000
11	-55.074	i[4]	address[6]	CLOCK_50	CLOCK_50	20.000
12	-55.061	i[31]	address[3]	CLOCK_50	CLOCK_50	20.000
13	-55.059	i[0]	address[5]	CLOCK_50	CLOCK_50	20.000
14	-55.045	i[0]	address[6]	CLOCK_50	CLOCK_50	20.000
15	-55.023	i[31]	address[2]	CLOCK_50	CLOCK_50	20.000
16	-55.010	i[6]	address[4]	CLOCK_50	CLOCK_50	20.000
17	-54.997	i[31]	address[1]	CLOCK_50	CLOCK_50	20.000

Slowest path is from bit 6 of the i register to bit 5 of the address input of s_mem

“Slack” is difference between “this path delay” and “target clock period” (20ns).
Negative slack is BAD. Often hear about “worst-case negative slack” or WCNS₁₁

What is this path?

Right click, Report-Worse-Case Path:

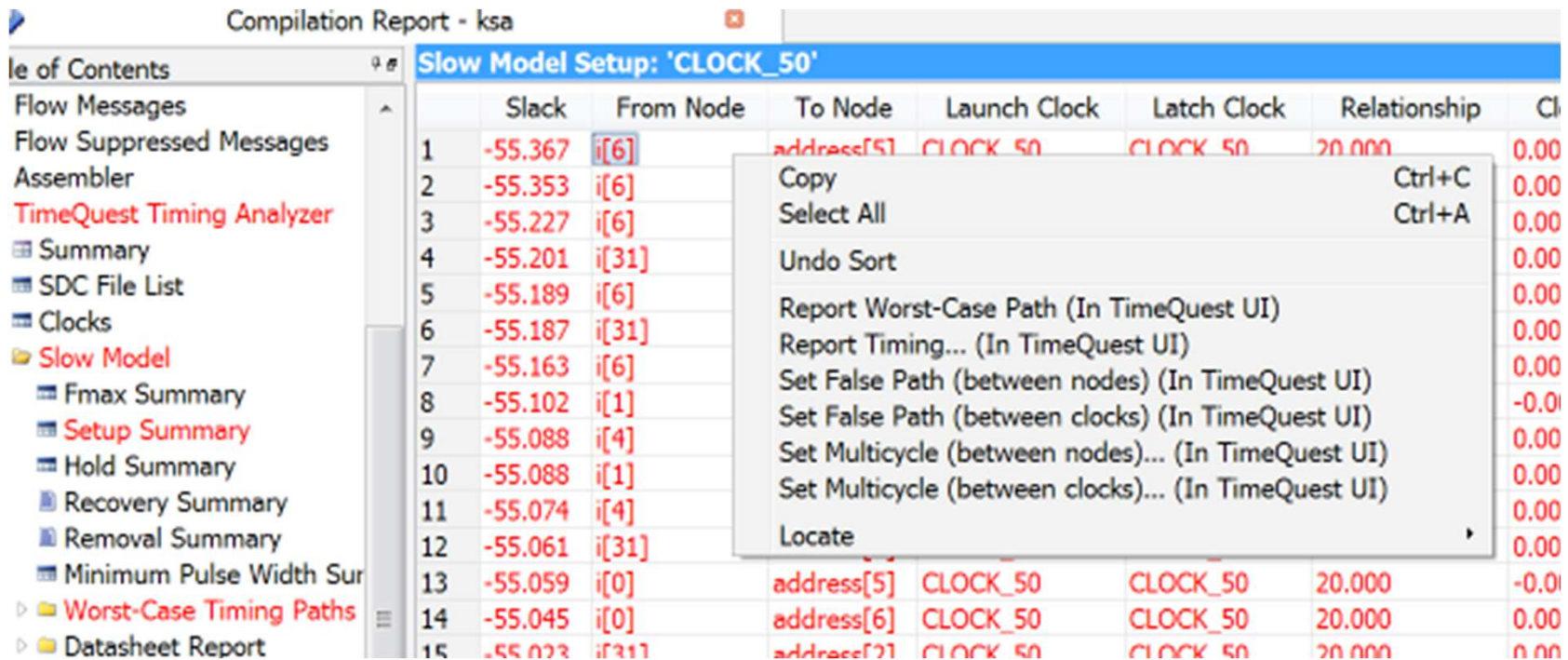

Compilation Report - ksa

Slow Model Setup: 'CLOCK_50'

	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Cl
1	-55.367	i[6]	address[5]	CLOCK_50	CLOCK_50	20.000	0.00
2	-55.353	i[6]					0.00
3	-55.227	i[6]					0.00
4	-55.201	i[31]					0.00
5	-55.189	i[6]					0.00
6	-55.187	i[31]					0.00
7	-55.163	i[6]					0.00
8	-55.102	i[1]					-0.00
9	-55.088	i[4]					0.00
10	-55.088	i[1]					0.00
11	-55.074	i[4]					0.00
12	-55.061	i[31]					0.00
13	-55.059	i[0]	address[5]	CLOCK_50	CLOCK_50	20.000	-0.00
14	-55.045	i[0]	address[6]	CLOCK_50	CLOCK_50	20.000	0.00
15	-55.033	i[31]	address[2]	CLOCK_50	CLOCK_50	20.000	0.00

Can go into Timing Quest and select Create Timing Network and then come back...

ath #1: Setup slack is -55.367 (VIOLATED)

Path Summary

Statistics

Data Path

Waveform

ata Arrival Path

	Total	Incr	RF	Type	Fanout	Location	Element
	0.000	0.000					launch edge time
↙	2.755	2.755					clock path
	2.755	2.755	R				clock network delay
↙	78.165	75.410					data path
	3.005	0.250		uTco	1	LCFF_X42_Y25_N17	i[6]
	3.005	0.000	RR	CELL	7	LCFF_X42_Y25_N17	i[6] regout
	3.527	0.522	RR	IC	1	LCCOMB_X41_Y25_N26	Mod0 auto_generated div...bs_num cs1a[6]~21 dataa
	3.940	0.413	RR	CELL	1	LCCOMB_X41_Y25_N26	Mod0 auto_generated di...num cs1a[6]~21 combout
	4.215	0.275	RR	IC	1	LCCOMB_X41_Y25_N2	Mod0 auto_generated div...bs_num cs1a[6]~22 datab
	4.608	0.393	RR	CELL	4	LCCOMB_X41_Y25_N2	Mod0 auto_generated di...num cs1a[6]~22 combout
	4.870	0.262	RR	IC	1	LCCOMB_X41_Y25_N16	Mod0 auto_generated div...bs_num cs1a[8]~23 datad

ata Required Path

It is coming out of register i and going to a divider...

Combinational dividers are notoriously slow...

Look at the code to see what is happening...

In my code, I found something like:

```
state_main_1: begin
    i = (i + 1) % 256;
    wren <= 1'b0;
    address <= i[7:0];    // read s[i]
    state <= state_main_2;
```

I suspect the division might be due to this mod function. But, of course, mod 256 is really just taking the 8 order LSB. We could get rid of that and just remove the % 256.

So, I do it and recompile...

Compilation Report - ksa

ksa.v

Contents

- Summary
- Settings
- Non-Default Global Settings
- Elapsed Time
- OS Summary
- Log
- Synthesis & Synthesis

Messages

- Suppressed Messages
- Compiler
- Quest Timing Analyzer
- Summary
- File List
- Checks
- Slow Model
- Slow Model Fmax Summary
- Setup Summary
- Hold Summary
- Recovery Summary
- Removal Summary

Slow Model Fmax Summary

	Fmax	Restricted Fmax	Clock Name	Note
1	13.45 MHz	13.45 MHz	CLOCK_50	

It didn't help!

You are beginning to understand why engineers find timing closure so challenging...



Going back to my code, I see:

```
state_swap_3: begin
    oldsi = q; // s[i] is now available
    j = ( j + q + secret_key[i%3]);
    // ...
```

Certainly if we are dividing by 3, this should be a small enough circuit right?

But wait.... in my implementation, i is an integer (32 bits) and the constant 3 is interpreted as 32 bits. So this constructs a 32 bit divider!



So, replace it with this:

```
state_swap_3: begin
    oldsi = q; // s[i] is now available
    j = ( j + q + secret_key[i%3]);
    // read s[j]
```



```
state_swap_3: begin
    oldsi = q; // s[i] is now available
    j = ( j + q + secret_key[i[7:0]%2'b11]);
    // read s[j]
```

Then recompile and ...

Report - ksa

ksa.v

Slow Model Fmax Summary


	Fmax	Restricted Fmax	Clock Name	Not
1	59.29 MHz	59.29 MHz	CLOCK_50	

Global Settings

Messages

Analyzer

That did it!



That was a case study to introduce you to the ~~frustrations~~ concept of timing closure.

Can Go Faster Than Predicted Fmax?

Overclocking

- Quartus gives conservative estimate
- Actual delays vary chip-to-chip


Dangerous... don't do it

- In testing, it might appear to work.
But, how do you know that you are exercising the critical path?
- Some chips will be slower than the one used for prototyping
- Conditions such as temperature can affect gate delays



PIPELINING

From earlier: Critical Path Delay


 



Critical Path is

$B \rightarrow \text{AND} \rightarrow \text{INV} \rightarrow \text{OR} \rightarrow \text{OR} \rightarrow \text{AND} \rightarrow X$

Critical Path Delay is 5ns

  Clock period cannot be smaller than 5ns or else X register will read in wrong data



 

The new longest path between registers is 3 ns.


So, this now goes at $1/3\text{ns} = 333\text{ MHz}$ (before it was $1/5 = 200\text{ MHz}$)

But it takes 2 cycles to get a result now.

Have we really improved anything?

Pipelining might help if:

 
1. One (or several) of the paths are very long, compared to the others. In that case, these slow paths dictate performance. If we pipeline the slow parts, we can run the whole circuit faster.
2. We can sometimes have multiple data items “in flight” at once:



Limits to pipelining

There is a limit to how much benefit you can get from pipelining:

 - Every pipeline stage has the overhead of $t_{\text{clk_to_q}}$ and t_{setup} .



In an FPGA it can be even worse.

In some FPGAs, signal must pass through extra interconnect and a LUT just to use the flip-flop.

Pipelining changes the timing behaviour of your circuit

- Need to take this into account when you are designing your datapath + controller


Quartus II will **not** pipeline your circuit for you. Why?

- Synthesis tools are “cycle accurate”: the behaviour of the circuit must be the same, cycle-by-cycle, as the Verilog specification.
- Pipelining a design would create a different cycle-by-cycle behaviour

Hyper-Pipelining in Stratix 10

Most recent device family has an optional **flip-flop at every switch** in the routing.

 NOTE: can't use reset on these FFs (design should avoid use of resets)




Important Point: Modern FPGAs support very fast clock speeds and heavily pipelined architectures. Lots of registers.

RETIMING


Retiming

Key to pipelining: make every stage balanced (same delay)


To balance, may need to move gates:

 

Max Freq =
 $1/4\text{ns} =$
250 MHz

 

Max Freq =
 $1/3\text{ns} =$
333 Mhz

 

This increased my Fmax from 59 MHz to 76 MHz !!
(...not always successful...)

Compilation Report - ksa

ksa.v

Assignment Editor

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Fitter
 - Flow Messages
 - Flow Suppressed Messages
- Assembler
- TimeQuest Timing Analyzer**
 - Summary
 - SDC File List
 - Clocks
 - Slow Model
 - Fast Model
 - Multicorner Timing Analysis Sur
 - Multicorner Datasheet Report S


Slow Model Fmax Summary

	Fmax	Restricted Fmax	Clock Name	Note
1	75.67 MHz	75.67 MHz	CLOCK_50	

Initial Value Problem with Re-timing:

Forward Re-Timing:

Each of these have an initial value

 


What is the initial value of R4?

Can Quartus determine it automatically?

Yes, eg simulate combinational logic with initial values of R1,R2,R3.

Initial Value Problem with Re-timing:

Backward Re-Timing:

 


What is initial value of Rb, Rc, and Rd?
(given the initial value of Ra specified by the user)

No. Simulation doesn't work "backwards". Must go through all combinations of Rb, Rc, and Rd to determine which combination gives Ra.


So: Initial values for registers may limit opportunities for retiming.

Clock Skew

 

Alpha 21164 (EV5)

Clock Skew in Alpha Processor

 

© Prentice Hall

Clock Skew


Clock Skew is very real:

- We can not guarantee that the clock edge arrives at all flip-flops at the same time

Implications:

- Improvement in F_{max} (very unlikely)
- Reduction in F_{max}
- Failure of the design, regardless of F_{max}

Clock Skew

 

If D is 0 (no skew), we know from the previous slide set that:

$$t_{\text{clock}} \geq t_{\text{clk_to_q}} + t_{\text{logic}} + t_{\text{setup}}$$

What if $D > 0$ (clock skew)?

$$t_{\text{clock}} + D \geq t_{\text{clk_to_q}} + t_{\text{logic}} + t_{\text{setup}}$$


Or:

$$t_{\text{clock}} \geq t_{\text{clk_to_q}} + t_{\text{logic}} + t_{\text{setup}} - D$$

In this case, clock skew
increased our clock frequency!

Analogy

Suppose this is your course schedule:

 

Nominally, you have **10 minutes** to get from one class to the other.


But, if next prof's watch is 2 minutes late, you have **12 minutes** to get there.

What if next prof's watch is 2 minutes early?



You've only got **8 minutes!**

Clock Skew

 


$$t_{\text{clock}} - D \geq t_{\text{clk_to_q}} + t_{\text{logic}} + t_{\text{setup}}$$

Or:

$$t_{\text{clock}} \geq t_{\text{clk_to_q}} + t_{\text{logic}} + t_{\text{setup}} + D$$

 In this case, clock skew
decreased our clock frequency!



In this case, the minimum clock period:

- decreases due to top path
- increases due to bottom path


Since the critical path is the **worst case path**:

$$t_{\text{clock}} \geq t_{\text{clk_to_q}} + t_{\text{logic}} + t_{\text{setup}} + D$$

ie. Overall, the clock skew increases the critical path (slows us down)

Clock Skew

 Clock skew can also cause hold time violations:




Tool needs to check for the worst case skew when checking hold time violations.

To fix, it increases routing delay to B.


suppose B arrives *just* late enough to avoid a hold time violation

what if CLKB is *delayed* with respect to CLKA?


Hold time example:

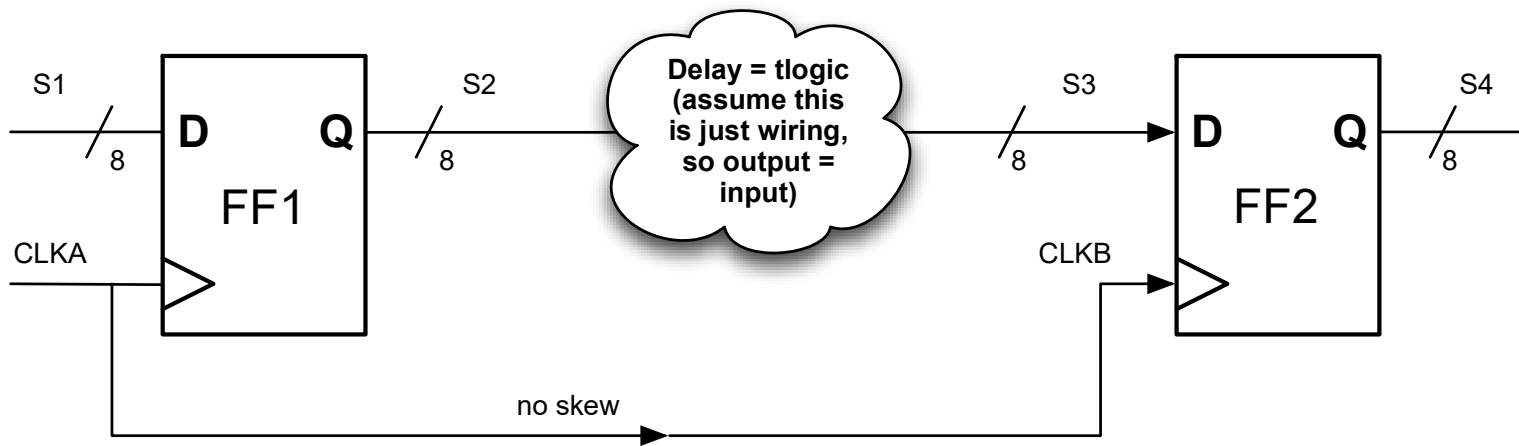


Correct Operation
(no skew)

 

Hold time example:

 


Correct Operation
(no skew)

 


FF1 Latches 46
@ edge 1

Hold time example:

 


Correct Operation
(no skew)

 


FF1 Latches 46
@ edge 1

FF2 Inputs 45
@ edge 1

Hold time example:

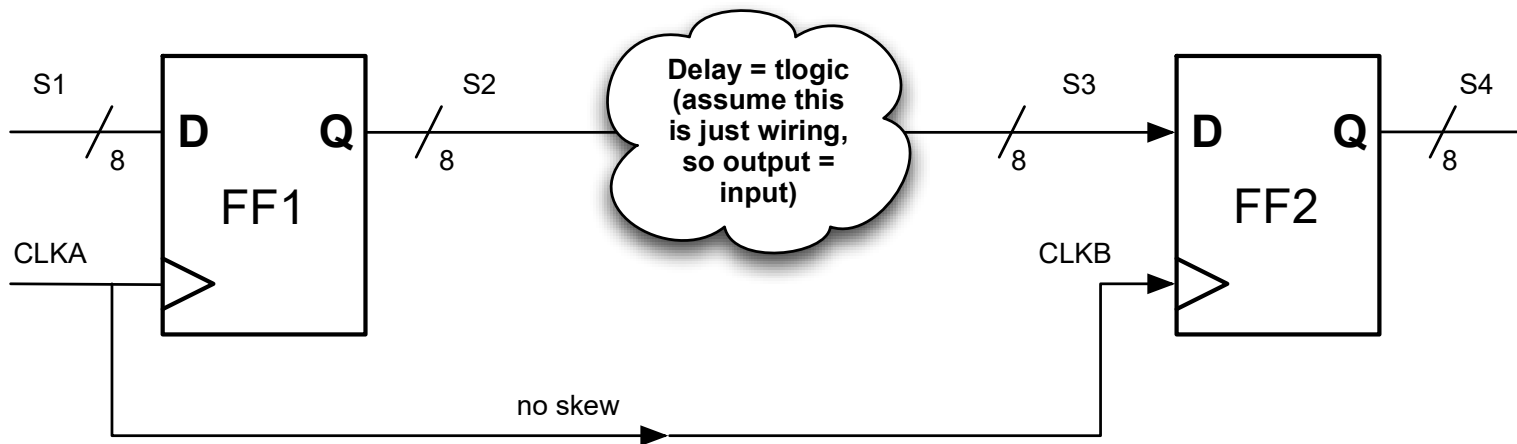

Correct Operation
(no skew)

 


FF1 Latches 46
@ edge 1


FF2 Inputs 45
@ edge 1

FF2 Latches 45
@ edge 1


Now suppose there is skew:

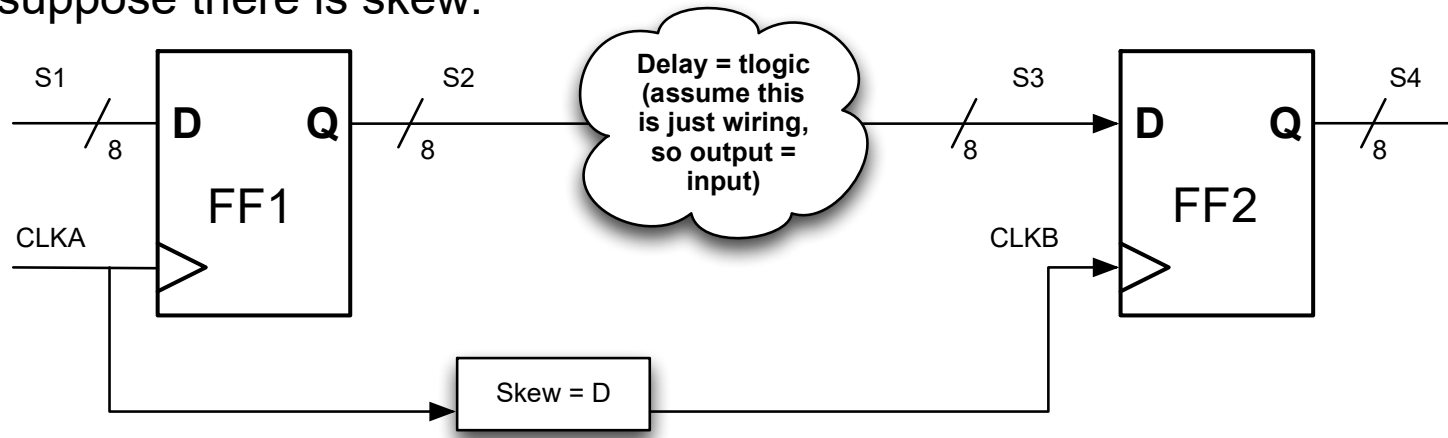


Now suppose there is skew:

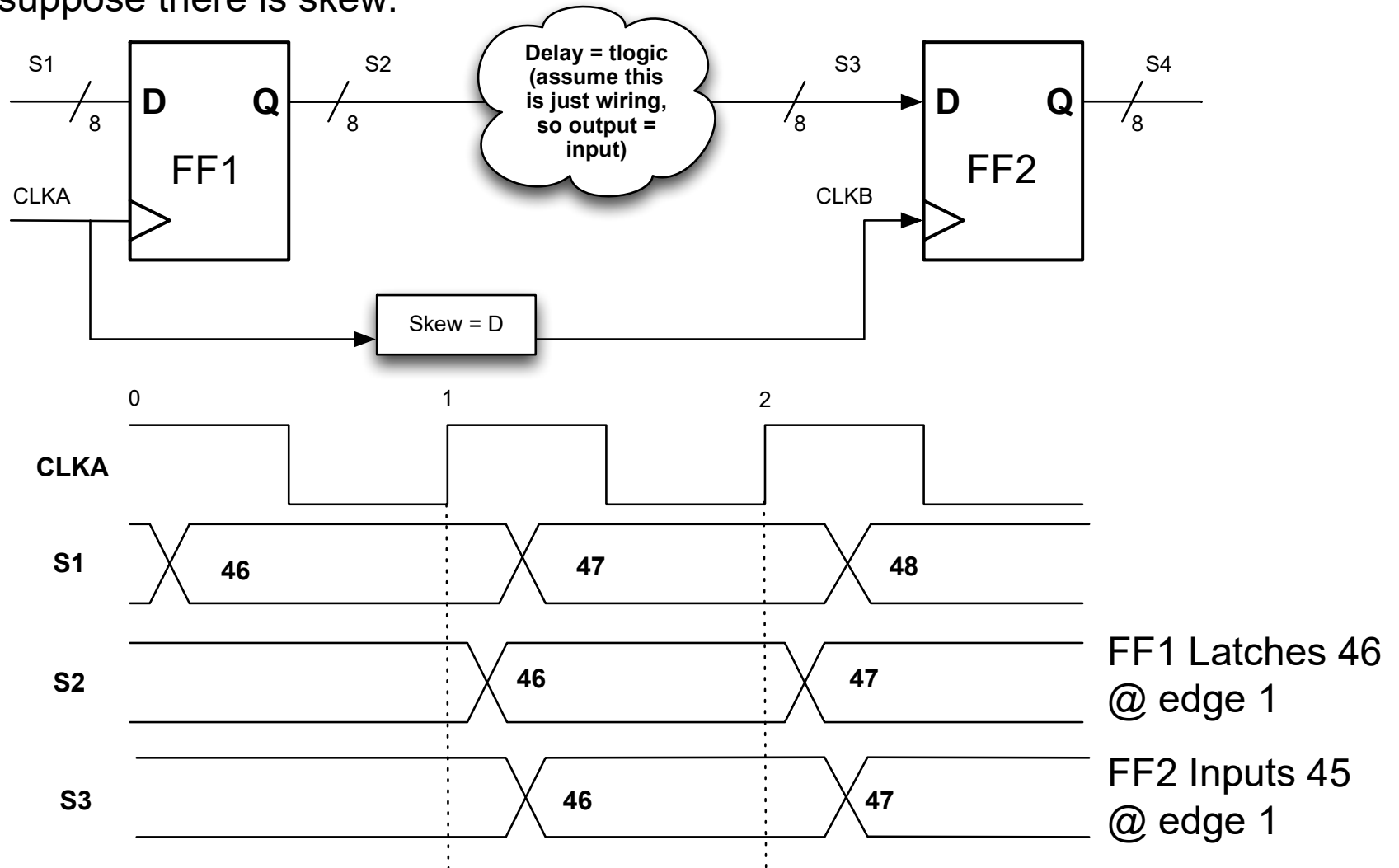


Now suppose there is skew:

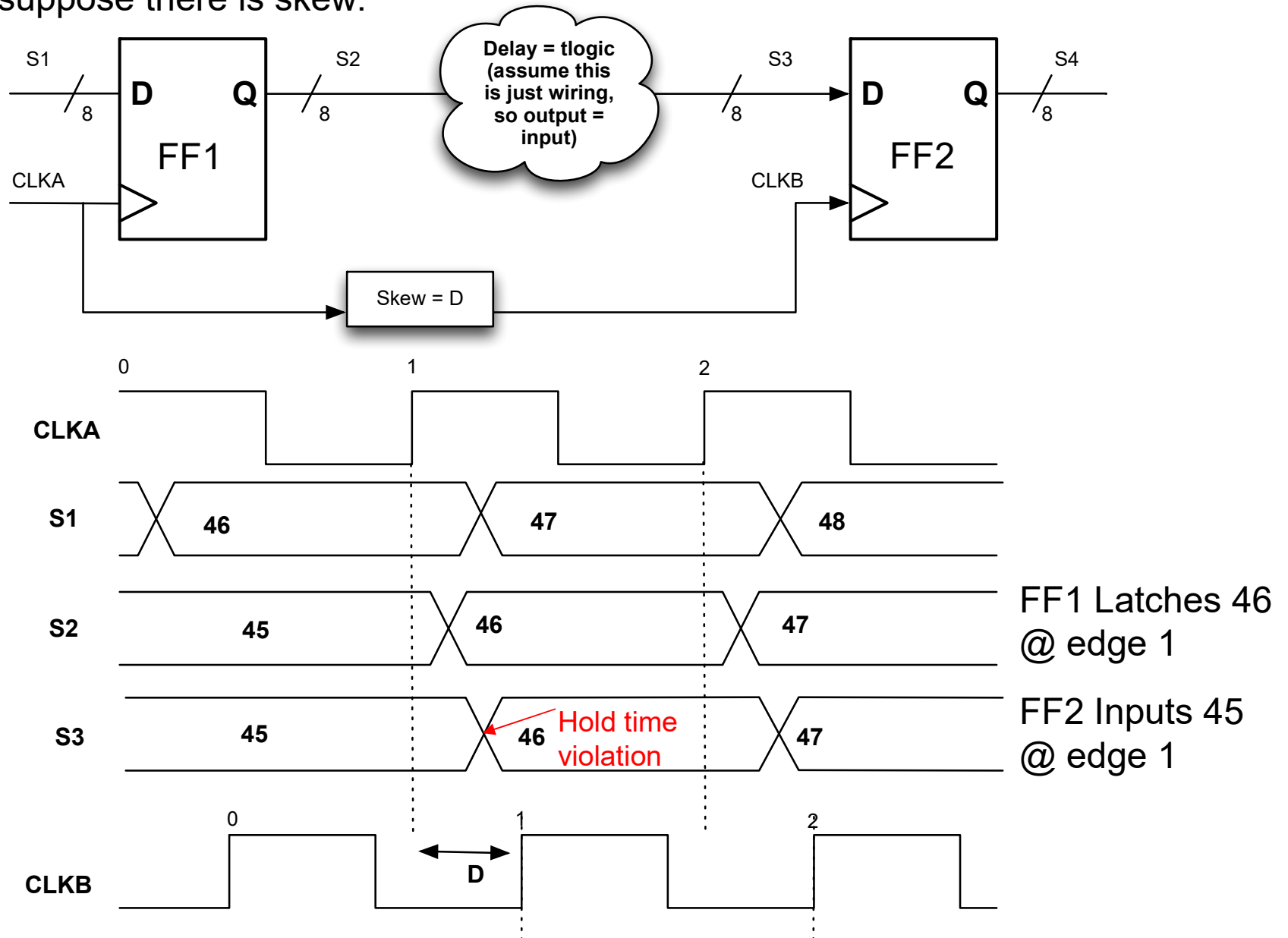

Now suppose there is skew:

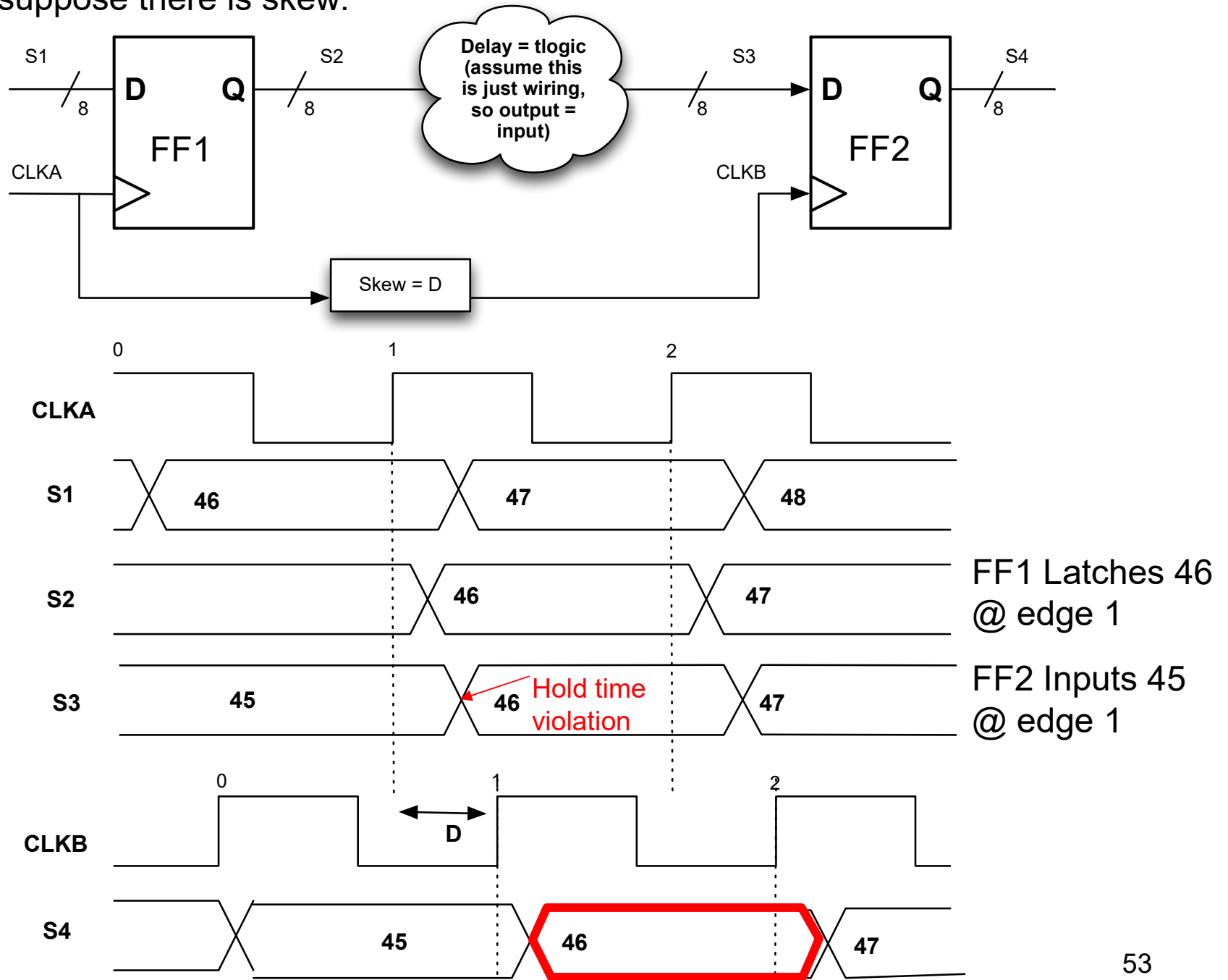

Now suppose there is skew:

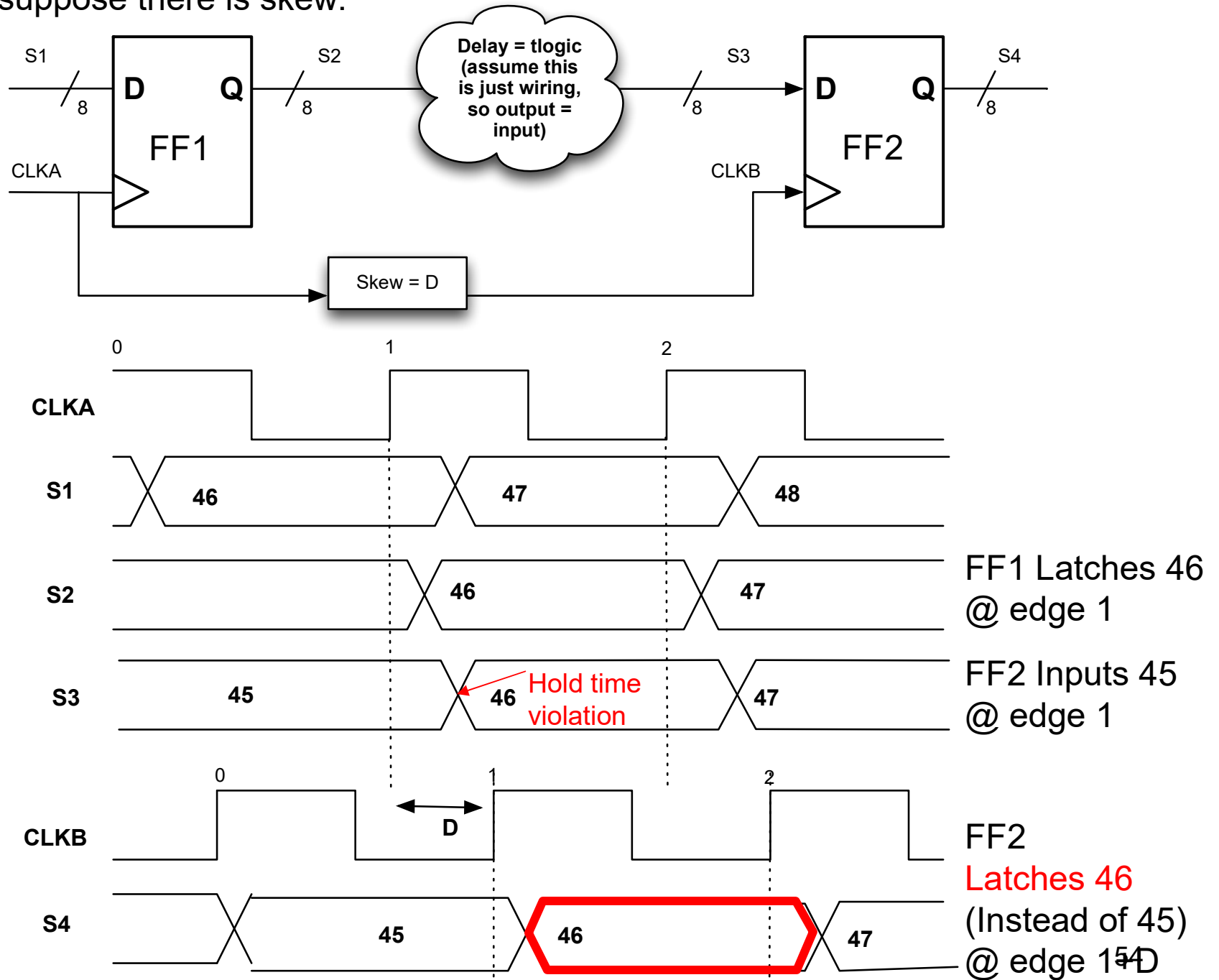


In this example, skew caused a hold violation, causing the second value “46” to race through too early. This caused a functional violation.

Slowing the clock speed doesn't help.

Lesson: Clock skew needs to be avoided as much as possible

Clock Skew: What can we do? Custom Chip

 

CLOCK


H-Tree Network

Observe: Only Relative Skew is Important

Layout clock signal to
minimize skew

Need to verify timing
extensively to make sure
skew is not going to cause
failure.

Clock Skew: FPGAs

 


FPGAs have complex clock distribution networks to achieve low skew

CAD tools must verify against clock skew problems.

PLLs: Motivation

Consider the VGA core from earlier lab:

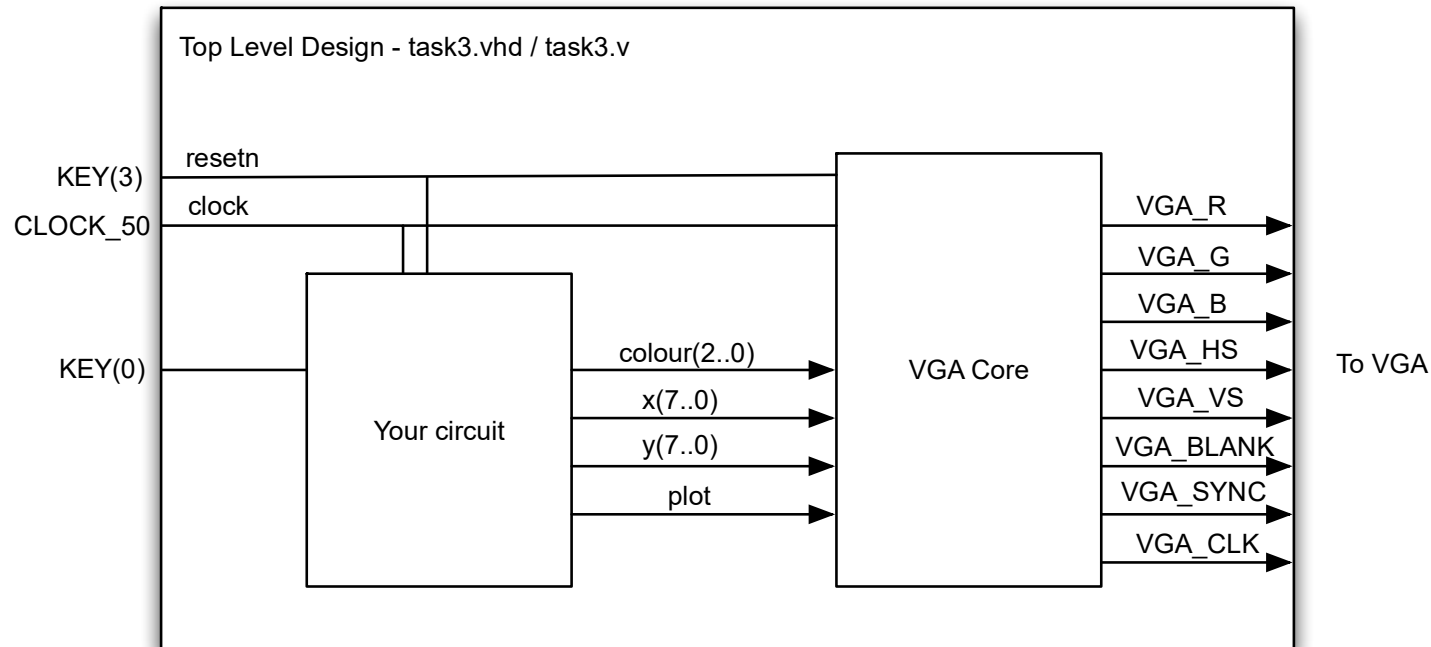

Your chip receives a 50 MHz clock

The VGA spec says VGA_CLK needs to run at 25 MHz*


The designer of the VGA core had to make a 25MHz clock out of a 50MHz clock

PLLs: Motivation

How would you make a circuit that creates a 25 MHz clock from a 50 MHz clock?



PLLs: Motivation

 How would you make a circuit that creates a 25 MHz clock from a 50 MHz clock?



PLLs: Motivation

  
How would you make a circuit that creates a 25 MHz clock from a 50 MHz clock?



PLLs: Motivation

Two problems with this solution:

 1. Clock skew between CLOCK_50 and CLOCK_25
2. Even if you use only CLOCK_25, it must be distributed across the entire chip. FPGA routing is slow and unpredictable.




Even if CLOCK_25 uses the global clock distribution network, we still have to route from our FF output to the source of these wires.


Phase Locked Loops

Modern FPGAs contain Phase Locked Loop hard cores:

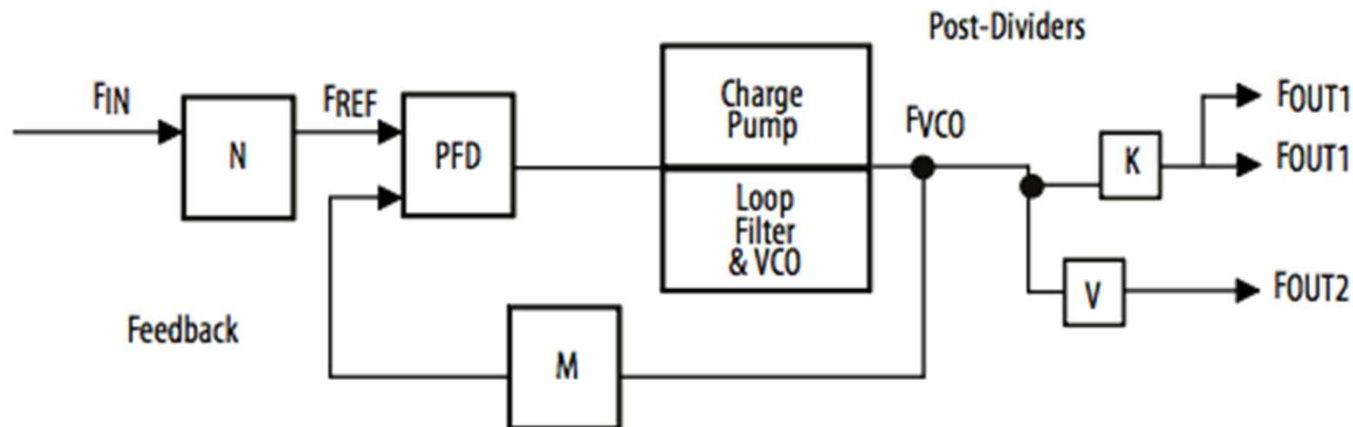- A mixed-signal circuit (= both analog and digital) that generates output clocks aligned to an input clock
- Can act as a clock speed divider or multiplier
- Can directly feed clock distribution network
- Automatically adjusts phase to account for clock distribution network



Cyclone V PLL: Detail

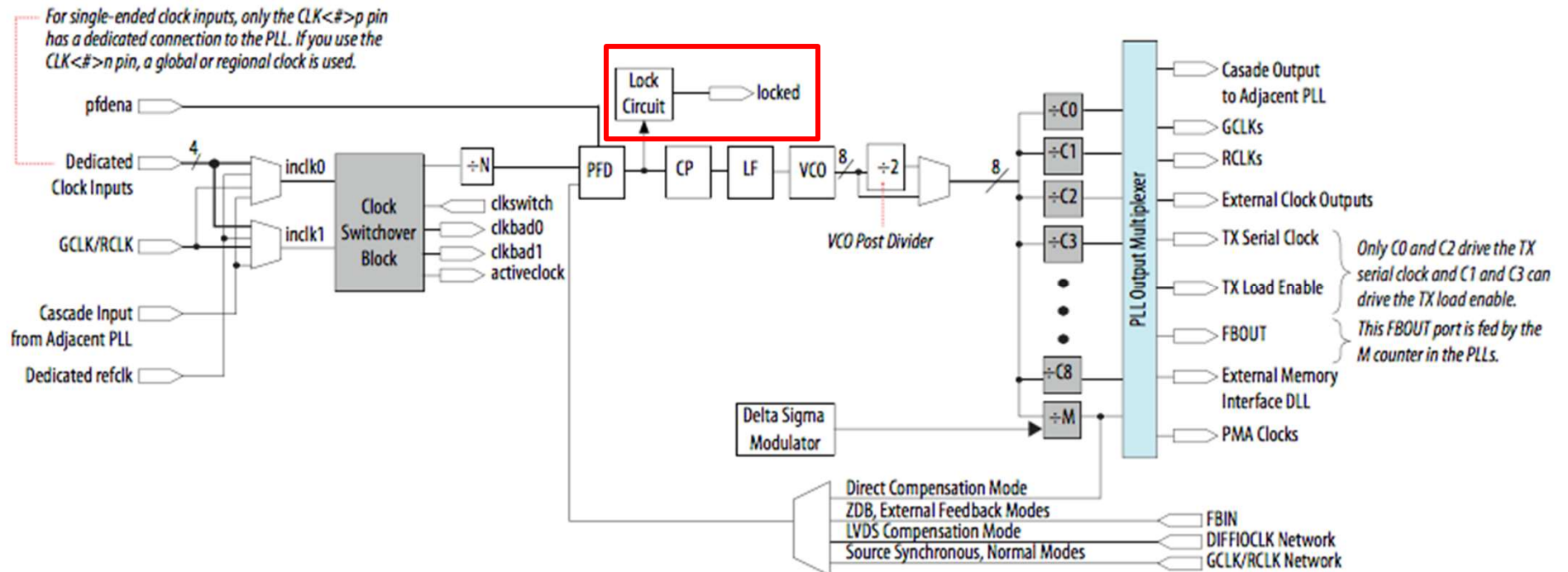

From Cyclone V Handbook

Phase Locked Loops

If you look inside vga_pll.v and vga_adapter.v :

```
altpll altpll_component (.inclk (clock_input_bus),
    .clk (clock_output_bus));
defparam
    altpll_component.operation_mode = "NORMAL",
    altpll_component.intended_device_family = "Cyclone
II",

    altpll_component.lpm_type = "altpll",
    altpll_component.pll_type = "FAST",
    altpll_component.inclclk0_input_frequency = 20000,
    altpll_component.primary_clock = "INCLK0",
    altpll_component.compensate_clock = "CLK0",
    altpll_component.clk0_phase_shift = "0",
    altpll_component.clk0_divide_by = 2,
    altpll_component.clk0_multiply_by = 1,
```

```
vga_pll mypll (CLOCK_50, clock_25);
```

Used to divide the clock frequency by 2. Can also multiply clock frequency. Don't worry about details. If you ever need it, you can look it up

Many PLL Parameters

General

Which device speed grade will you be using?

☐ Use military temperature range devices only

What is the frequency of the inlock0 input?

☒ Set up PLL in LYDS mode Data rate:

Lock output

☒ Create 'locked' output

☒ Enable self-reset on loss of lock

Operation mode

How will the PLL outputs be generated?

☒ Use the feedback path inside the PLL

☐ In Normal Mode

☐ In Source-Synchronous Compensation Mode

☒ In Zero Delay Buffer Mode

☐ Connect the fbmimic port (bidirectional)

☐ With no compensation

☐ Create an 'fbin' input for an external feedback (External Feedback Mode)

Which output clock will be compensated for?

c0 - Core/External Output Clock

Cannot implement the requested PLL
Cause: Requested mult/div factors not achievable

☒ Use this clock

Clock Tap Settings

	Requested settings	Actual settings
<input type="radio"/> Enter output clock frequency:	<input type="text" value="100.0000000"/> <input type="text" value="MHz"/>	<input type="text" value="20.0000000"/>
<input checked="" type="radio"/> Enter output clock parameters:		
Clock multiplication factor	<input type="text" value="205"/>	<input type="text" value="1"/>
Clock division factor	<input type="text" value="1025"/> << Copy	<input type="text" value="5"/>
Clock phase shift	<input type="text" value="0.75"/> <input type="text" value="deg"/>	<input type="text" value="0.56"/>
Phase shift step resolution(ps)		
Clock duty cycle (%)	<input type="text" value="50.00"/>	<input type="text" value="50.00"/>

Note: The displayed internal settings of the PLL is recommended for use by advanced users only

Description	Value
Primary clock VCO frequency (MHz)	1600.000
Modulus for M counter	16
Modulus for N counter	1
Initial VCO phase cycles for M counter	1
VCO phase tap for M counter	0
VCO post scale counter	1

c0 settings:

☐ Use these clock settings for the DPA clock
(For the Left-Right PLL type only)

Per Clock Feasibility Indicators

c0 c1 c2 c3 c4 c5

c5

(parameter values shown are just examples, not recommendations)

Glitches


Glitch

An undesired short-lived pulse that occurs before a signal settles to its intended value


Causes

- Unequal arrival times of inputs on combinational gates
- Various electrical effects (eg crosstalk, not covered in this course)


Example of a circuit with glitching:

 

Glitch Example

 

B	C	D
0	0	0
0	1	1
1	0	1
1	1	0

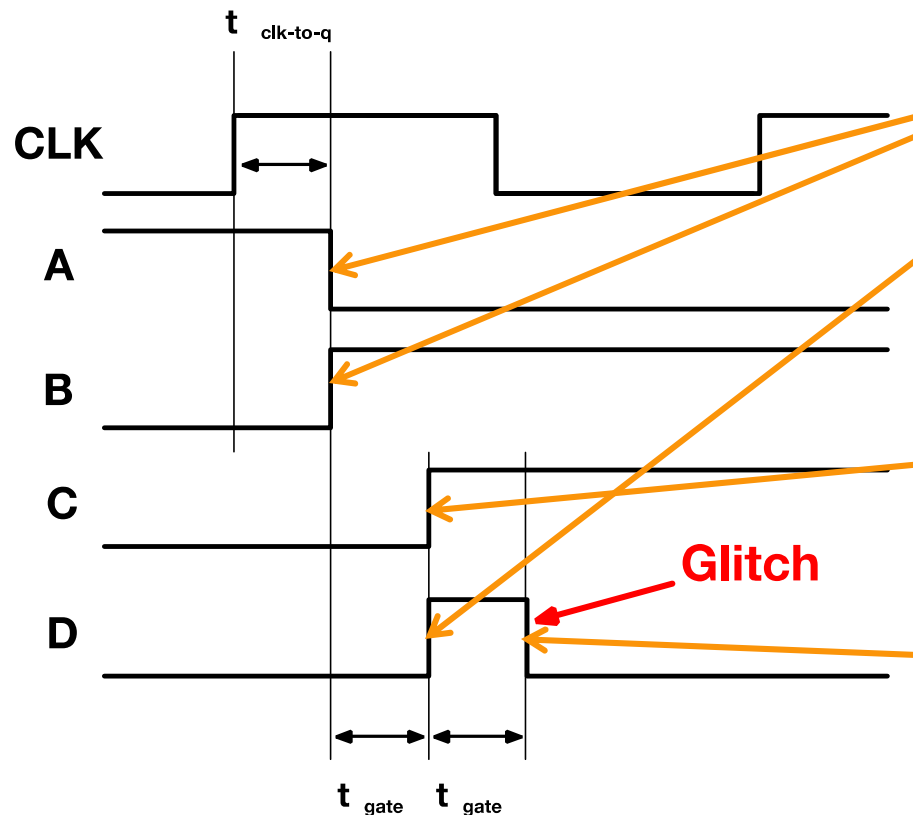

1) A, B settle after clock-to-q delay

2a) B arrives immediately at XOR, causing a transition to 1 on D after one gate delay

2b) At the same time, A arrives at the INV immediately, causing a transition to 1 on C after one gate delay

3) After C settles, its value arrives at the XOR after one additional gate delay, causing a transition back to 0 on D

Glitches – Key Take Aways

A signal may switch several times before settling to final intended value

- Source (new glitch): uneven signal arrival times on inputs
- Propagate (existing glitch): input glitch → output glitch

Glitches are normal ...

ok if signal is stable before anyone tries to do something with data
eg, before t_{setup} of flip-flop

Power and Energy

- Glitches cause extra charge/discharge cycles of output capacitance
- Unnecessary power consumption

Learning Objectives

1. Understand what timing closure is and why it is difficult
2. Understand how pipelining can help with timing closure
3. Understand retiming and be able to apply it to a circuit
4. Be able to discuss the effects of clock skew
5. Understand what a PLL is used for
6. Understand the cause and impact of glitches caused by unequal combinational path delays